



ASSIGNMENT-1

Digital System Design

Name: - Nirbhay Thakkar

ID: - 21EL092

Course Code: - 3EL41

Q1) Write a Verilog code for 2X4 decoder


Design :-

```
module decoder(  
    input a,b,en;  
    output[3:0] y;  
);  
    wire enb,na,nb;  
  
    assign enb = ~en;  
    assign na = ~a;  
    assign nb = ~b;  
    assign y[0] = ~(na&nb&enb);  
    assign y[1] = ~(na&b&enb);  
    assign y[2] = ~(a,nb,enb);  
    assign y[3] = ~(a,b,enb);  
  
endmodule
```

Testbench :-

```
module tb;  
  
    reg a,b,en;  
    wire [3:0]y;  
  
    decoder24_assign dut(en,a,b,y);  
    initial begin  
        $dumpvars;  
        $dumpfile("dump.vcd");  
        $monitor("en=%b a=%b b=%b y=%b",en,a,b,y);  
  
        en=1;a=1'bx;b=1'bx;#5  
        en=0;a=0;b=0;#5  
        en=0;a=0;b=1;#5  
        en=0;a=1;b=0;#5  
        en=0;a=1;b=1;#5  
  
        $finish;  
    end  
endmodule
```

Output :-

 

Q2) Write a Verilog code for Full subtractor


Design :-

```
module full_subtractor(input a, b, Bin, output D, Bout);
    assign D = a ^ b ^ Bin;
    assign Bout = (~a & b) | ~(a ^ b) & Bin;
endmodule
```

Testbench :-

```
module tb_top;
    reg a, b, Bin;
    wire D, Bout;
    full_subtractor fs(a, b, Bin, D, Bout);
    initial begin
        $monitor("At time %0t: a=%b b=%b, Bin=%b, difference=%b, borrow=%b", $time,
            a, b, Bin, D, Bout);
        a = 0; b = 0; Bin = 0; #1;
        a = 0; b = 0; Bin = 1; #1;
        a = 0; b = 1; Bin = 0; #1;
        a = 0; b = 1; Bin = 1; #1;
        a = 1; b = 0; Bin = 0; #1;
        a = 1; b = 0; Bin = 1; #1;
        a = 1; b = 1; Bin = 0; #1;
        a = 1; b = 1; Bin = 1;
    end
endmodule
```

Output :-

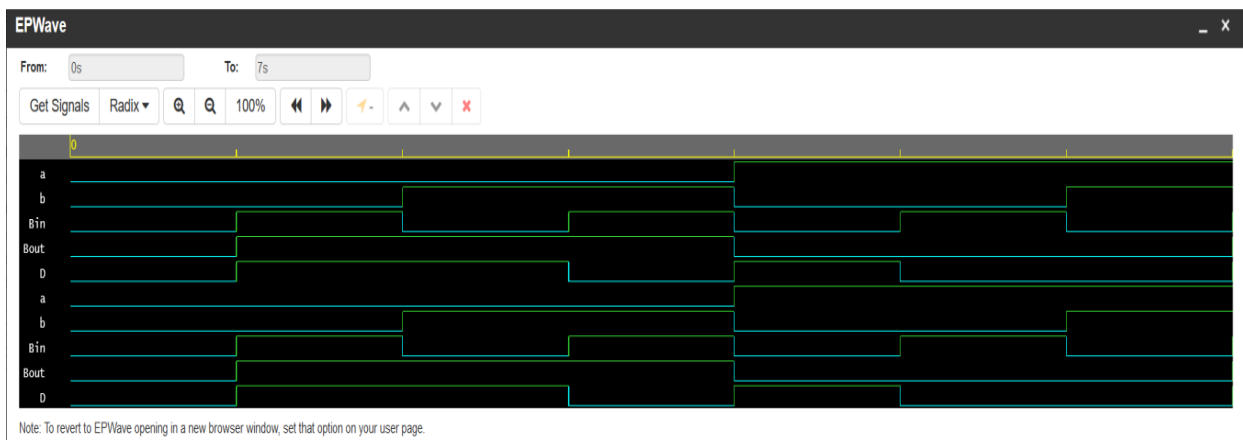

Q3) Write a Verilog code for 2-bit comparator

Design: -


```
module comparator(  
    input [1:0] A, B,  
    output reg A_grt_B, A_less_B, A_eq_B;  
    always@(*) begin  
        A_grt_B = 0; A_less_B = 0; A_eq_B = 0;  
        if(A>B) A_grt_B = 1'b1;  
        else if(A<B) A_less_B = 1'b1;  
        else A_eq_B = 1'b1;  
    end  
endmodule
```

Testbench: -

```
module tb;  
    reg [1:0] A, B;  
    wire A_grt_B, A_less_B, A_eq_B;  
    comparator comp(A, B, A_grt_B, A_less_B, A_eq_B);  
    initial begin  
        $dumpvars;  
        $dumpfile("dump.vcd");  
        $monitor("A = %0h, B = %0h -> A_grt_B = %0b, A_less_B = %0b, A_eq_B = %0b",  
            A, B, A_grt_B, A_less_B, A_eq_B);  
        repeat(5)  
            begin  
                A=$random; B=$random; #1;  
            end  
    end  
endmodule
```

SV/Verilog Testbench

Output: -

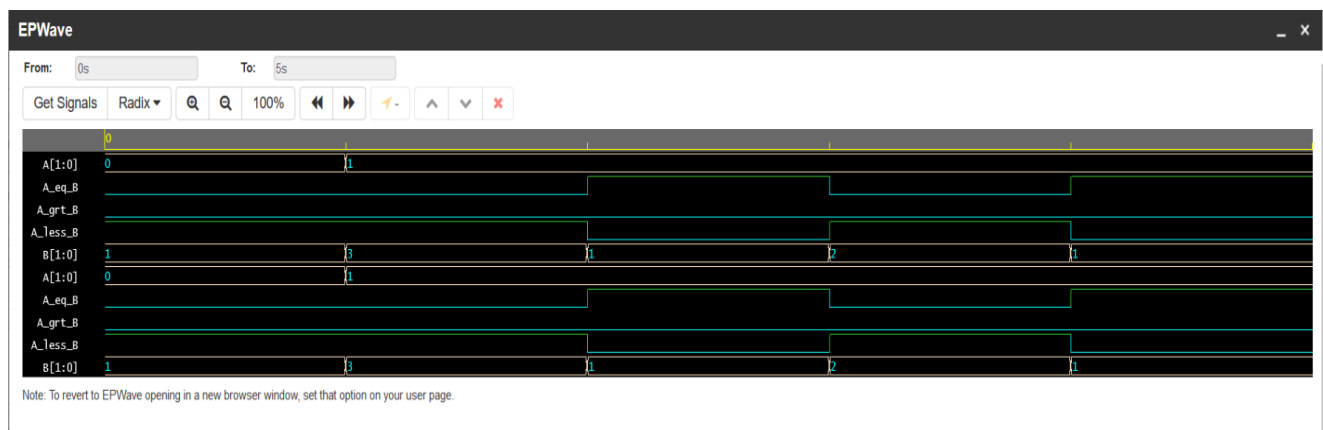

4) Write a Verilog code for 3 bit binary to gray convertor.


Design: -

```
module Binary_to_Gray(  
    input [3:0] b,  
    output [3:0] g  
);  
    assign g[0]=b[1]^b[0];  
    assign g[1]=b[2]^b[1];  
    assign g[2]=b[3]^b[2];  
    assign g[3]=b[3];  
  
endmodule
```

Testbench: -

```
module Binary_to_Gray_tb;  
    reg [3:0] b;  
    wire [3:0] g;  
    Binary_to_Gray uut (b,g);  
    initial begin  
        $dumpvars;  
        $dumpfile("dump.vcd");  
        b=4'b0000;  
        #10 b=4'b0001;  
        #10 b=4'b0010;  
        #10 b=4'b0011;  
        #10 b=4'b0100;  
        #10 b=4'b0101;  
        #10 b=4'b0110;  
        #10 b=4'b0111;  
        #10 b=4'b1000;  
        #10 b=4'b1001;  
        #10 b=4'b1010;  
        #10 b=4'b1011;  
        #10 b=4'b1100;  
        #10 b=4'b1101;  
        #10 b=4'b1110;  
        #10 b=4'b1111;  
    end  
endmodule
```

Output: -

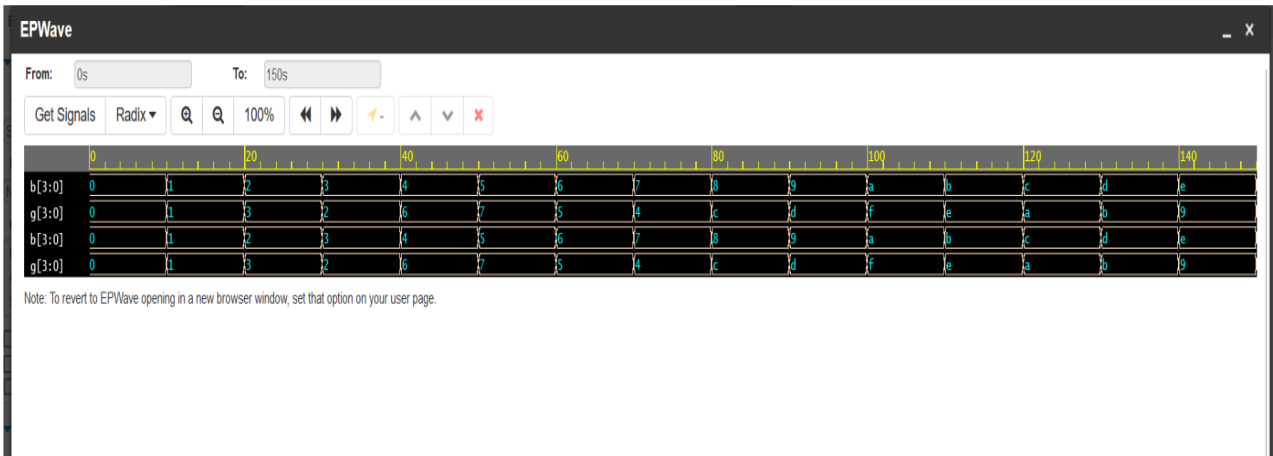

Q5) Write a Verilog code for BCD to excess 3 convertors.

Design: -

```
module Bcd_excess3(b,e);
    input [3:0] b;
    output [3:0] e;
    assign e[3]=b[3]|b[2]&b[1]|b[2]&b[0];
    assign e[2]=~b[2]&b[1]|~b[2]&b[0]|b[2]&~b[1]&~b[0];
    assign e[1]=b[1]&b[0]|~b[1]&~b[0];
    assign e[0]=~b[0];
endmodule
```

Testbench: -

```
module Bcd_excess3_tb;

    reg [3:0] b;
    wire [3:0] e;

    Bcd_excess3 uut (
        .b(b),
        .e(e)
    );
    initial begin
        $dumpvars;
        $dumpfile("dump.vcd");

        b=3'b0000;
        #10;
        b=4'b0001;
        #10;
        b=4'b0010;
        #10;
        b=4'b0011;
        #10;
        b=4'b0100;
        #10;
        b=4'b0101;
        #10;
        b=4'b0110;
        #10;
        b=4'b0111;
        #10;
        b=4'b1000;
        #10;
        b=4'b1001;
        #10;
        end
endmodule
```


Output: -

